

Queensland University of Technology

EGB120
Foundations of Electrical Engineering

Professor Geoff Walker

Dinal Atapattu

November 6, 2023

Contents

1	Circuits and Sources	3
1.1	Fundamental Electrical Quantities	3
1.2	Power and Energy	3
1.3	Circuits and Sources	3
1.4	Resistors and Ohm's Law	3
2	Filters and Rectifiers	4
3	Source Transformation	5
3.1	Thevenin Equivalent Circuits	5
3.2	Norton Equivalent Circuits	5
3.3	Superposition	5
3.4	Maximum Power Transfer	5
4	Ohm's Law, Kirchhoff's Laws, and Resistive Circuits	6
4.1	Kirchhoff's Laws	6
4.2	Series and Parallel Elements	6
4.3	Voltage and Current Dividers	6
4.4	Measuring Voltages and Currents	6
5	Diodes	7
5.1	Introduction to Diodes	7
5.2	Voltage and Current Characteristics	7
5.3	Operating Points and Load Lines	7
5.4	Practical Diodes	7
6	Mesh Analysis	8
6.1	Nodes, Loops, and Meshes	8
6.2	Mesh Analysis	8
6.3	Current Source Mesh Analysis	8
6.4	Dependant Source Mesh Analysis	8
7	Inductors and Capacitors	9
7.1	Capacitors	9
7.2	Inductors	9
7.3	Inductors and Capacitors in Steady State	9
8	RL and RC circuits and Time Response	10
8.1	Switches	10
8.2	Natural Response	10
8.3	Step Response	10
9	Operational Amplifiers	11
9.1	Introduction to Operational Amplifiers	11
9.2	Op Amp Analysis	11
9.3	Practical Op Amps	11
10	Sinusoidal State Analysis	12
10.1	Sinusoidal Signals	12
10.2	RMS	12
10.3	Phasors	12
10.4	Circuit Analysis with Phasors	12

11 Frequency Response of RL and RC Circuits	13
11.1 AC Circuit Analysis	13
11.2 Frequency Response and Transfer Functions	13
11.3 Bode Plots	13
12 Filters and Rectifiers	14
12.1 Filter Introduction	14
12.2 Passive Filters	14
12.3 Active Filters	14
13 Zener Diodes and Voltage Regulators	15
13.1 Rectifiers and Regulators	15
13.2 Zener Diode Regulators	15
13.3 Series Regulators	15
13.4 Op Amps as Regulators	15

Chapter 1

Circuits and Sources

1.1 Fundamental Electrical Quantities

1.2 Power and Energy

1.3 Circuits and Sources

1.4 Resistors and Ohm's Law

Chapter 2

Filters and Rectifiers

Chapter 3

Source Transformation

3.1 Thevenin Equivalent Circuits

3.2 Norton Equivalent Circuits

3.3 Superposition

3.4 Maximum Power Transfer

Chapter 4

Ohm's Law, Kirchoff's Laws, and Resistive Circuits

4.1 Kirchoff's Laws

4.2 Series and Parallel Elements

4.3 Voltage and Current Dividers

4.4 Measuring Voltages and Currents

Chapter 5

Diodes

5.1 Introduction to Diodes

5.2 Voltage and Current Characteristics

5.3 Operating Points and Load Lines

5.4 Practical Diodes

Chapter 6

Mesh Analysis

6.1 Nodes, Loops, and Meshes

6.2 Mesh Analysis

6.3 Current Source Mesh Analysis

6.4 Dependant Source Mesh Analysis

Chapter 7

Inductors and Capacitors

7.1 Capacitors

7.2 Inductors

7.3 Inductors and Capacitors in Steady State

Chapter 8

RL and RC circuits and Time Response

8.1 Switches

8.2 Natural Response

8.3 Step Response

Chapter 9

Operational Amplifiers

9.1 Introduction to Operational Amplifiers

9.2 Op Amp Analysis

9.3 Practical Op Amps

Chapter 10

Sinusoidal State Analysis

10.1 Sinusoidal Signals

10.2 RMS

10.3 Phasors

10.4 Circuit Analysis with Phasors

Chapter 11

Frequency Response of RL and RC Circuits

11.1 AC Circuit Analysis

11.2 Frequency Response and Transfer Functions

11.3 Bode Plots

Chapter 12

Filters and Rectifiers

12.1 Filter Introduction

12.2 Passive Filters

12.3 Active Filters

Chapter 13

Zener Diodes and Voltage Regulators

13.1 Rectifiers and Regulators

13.2 Zener Diode Regulators

13.3 Series Regulators

13.4 Op Amps as Regulators